

Digital Circuits Theory - Laboratory						
Academic year	Laboratory exercises on	Mode of studies	Field of studies	Supervisor	Group	Section
2020/2021	Wednesday	SSI	Informatics	KP	1	3
	16:30 – 18:15					

Report from Exercise No 3

Performed on: 14.10.2020

Exercise Topic: Bistable devices

Performed by:

Dawid Grobert

Purpose of the exercises

The aim of the tasks was to get to know the Flip-Flops – how they work and how to use them. It boiled down mainly to analyzing available flip-flops and describing them.

1 Description of the first task

Task 2

Recognise the triggering way of the synchronous D flip-flops (gated latch, master slave with or without 1s and 0s catching, or positive or negative edge-triggered). Draw timing charts used to resolve the problem.

1.1 Timing Chart

The only available flip-flop on my stand was D flip-flop. After plugging it in and testing, I got the following timing chart:

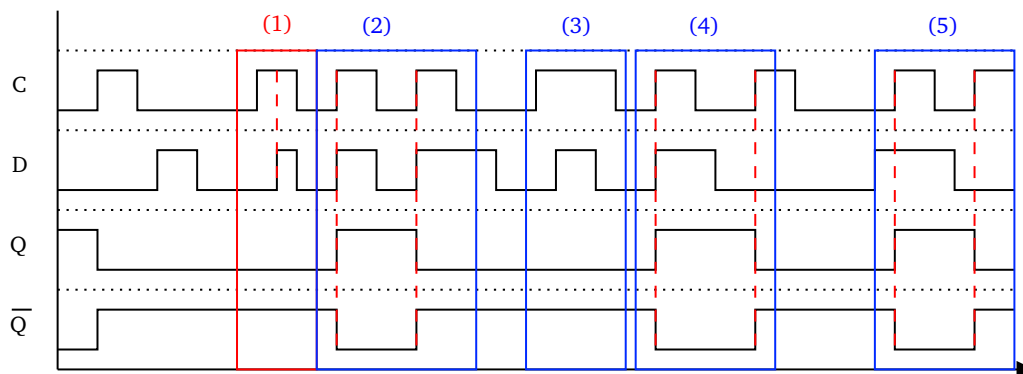


Figure 1: Timing Chart created during laboratory

- (1) A change in the middle of the high state of the clock has no effect.
- (2) Activating both the clock and D leads to a change of state. It is worth noting that this happens only for the positive edge, and no longer for the negative edge.
- (3) The digital circuit does not notice the change of D inside the high state of the clock. There is also no gated latch or 1s and 0s catching.
- (4) Again, activating D and the clock at the same time changes the state, but then activating the clock for low state D also changes the state of the output.
- (5) Finally, we can see that the changes are only noticeable on the positive edge of the clock – in the enclosed example, the clock notices a change of state D and changes the state on the output. It does the same thing moments later for a low state D.

1.2 Excitation Table

D	$Q^t \rightarrow Q^{t+1}$
0	$0 \rightarrow 0$
1	$0 \rightarrow 1$
0	$1 \rightarrow 0$
1	$1 \rightarrow 1$

The resulting timing chart clearly indicates that the flip-flop works according to the excitation table – and therefore works properly.

Table 1: Excitation Table of D flip flop

1.3 Answer

From the given timing chart I determined that the flip-flop is triggered by a positive edge. The change of the output signal occurs only when the corresponding D signal is changed from zero to one.

2 Description of the second task

Task 3

Use only asynchronous inputs of the synchronous D flip-flop to determine their active value and which of them is dominant. Draw timing charts used to resolve the problem

2.1 Timing Chart

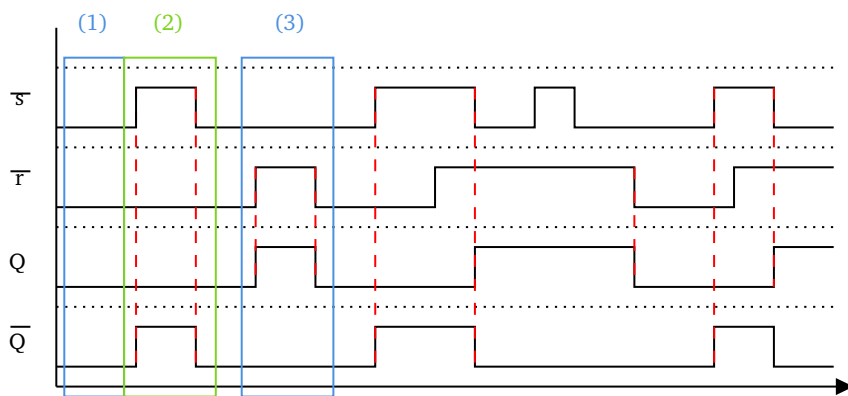


Figure 2: Timing Chart created during laboratory

- (1) Zeros on both inputs lead to zeroes on both Q and \bar{Q} inputs.
- (2) If the state is high on \bar{S} and low on \bar{R} , the output is high on \bar{Q} and low on Q .
- (3) A low on \bar{S} and a high on \bar{R} results in a high output on Q and a low on \bar{Q} .

2.2 Answer

We know that the reset is dominant, because for a high state \bar{S} and a high state \bar{R} the output Q gives zero. Their active values are zeroes.

3 Description of the third task

Task 5

For a flip-flop constructed as cross-coupled NANDs draw a timing chart illustrating the behaviour of the device. Basing on the chart determine the dominant input and the active level of both inputs.

3.1 The circuit

I started by connecting a digital circuit on my machine (see Fig 3).

 


Figure 3: Cross-coupled NAND

After connecting the digital circuit I went to tests to create a timing chart.

3.2 Timing Chart

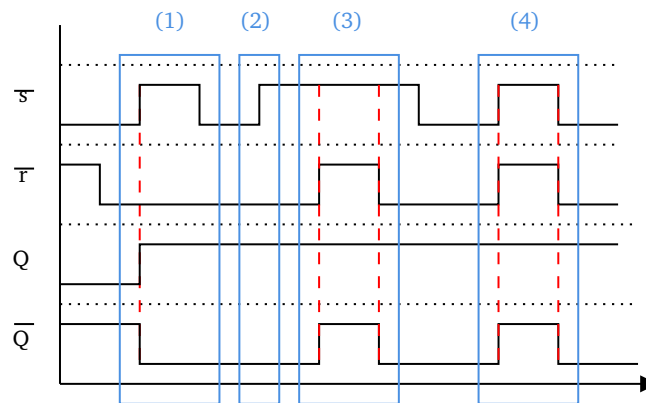


Figure 4: Timing Chart created during laboratory

- (1) We can see that the high state of the input \bar{s} made the output Q to change to 1 and \bar{Q} to 0.
- (2) Reactivating the input \bar{s} does not affect the output.
- (3) Enabling the input \bar{r} during a high state of \bar{s} has set \bar{Q} to high state.
- (4) Setting the inputs \bar{s} and \bar{r} to high again leads to high Q and \bar{Q} .

3.3 Truth Table

From the timing chart above (see Fig 4) we get:

S	R	Q
0	0	previous state
0	1	0
1	0	1
1	1	1 (set dominant)

Figure 5: Obtained truth table for the tested digital circuit.

3.4 Answer

From the truth table we can easily conclude that *set* is the dominant input. Active levels of both inputs are zeroes.

4 Description of the fourth task

Task 5

For a flip-flop constructed as cross-coupled NORs draw a timing chart illustrating the behaviour of the device. Basing on the chart determine the dominant input and the active level of both inputs.

4.1 The circuit

I started by connecting a digital circuit on my machine (see Fig 6).

 


Figure 6: Cross-coupled NOR

After connecting the digital circuit I went to tests to create a timing chart.

4.2 Timing Chart

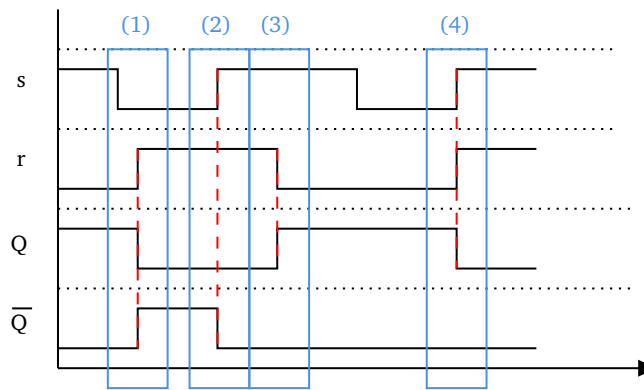


Figure 7: Timing Chart created during laboratory

- (1) We can see that r sets Q to 0 and \overline{Q} to 1.
- (2) When the r state is high, the s state got changed to high right after. This leads to a change in \overline{Q} from 1 to 0. This way both Q and \overline{Q} are zero.
- (3) When r is switched to low, only s is active and the result is $Q = 1, \overline{Q} = 0$
- (4) When the high state appeared again on two s and r signals at the same time, the result as before is the low state on both outputs.

4.3 Truth Table

Based on the timing chart above (see Fig 4) we get:

S	R	Q
0	0	previous state
0	1	0
1	0	1
1	1	0 (reset dominant)

Figure 8: Obtained truth table for the tested digital circuit.

4.4 Answer

From the truth table we can easily conclude that *reset* is the dominant input. Active levels of both inputs are ones.

5 Conclusions

During the labs, the exercises went exceptionally well. There were no anomalies and calm analysis of the tasks led to correct results. However, one of the main mistakes I made was that I didn't know how to treat on a timing-chart the variables that were negated.