

Digital Circuits Theory - Laboratory						
Academic year	Laboratory exercises on	Mode of studies	Field of studies	Supervisor	Group	Section
2020/2021	Wednesday	SSI	Informatics	KP	1	3
	15:30 – 17:00					

Report from Exercise No 6

Performed on: 28.10.2020

Exercise Topic: Selected arithmetic circuits

Performed by:

Dawid Grobert
Julia Boczowska

Purpose of the exercises

The aim of the exercise was to learn about such elements as: adder, comparator. More generally, we were dealing with arithmetic combinations and sequential systems performing arithmetic operations.

1 Description of the first task

Task 1

Using prepared by yourself test data (pairs of input values and the expected outcomes for the operation), verify the working mode of 4-bit adder with respect to the used representation of binary numbers, whether it adds numbers:

- with sign, in Sign-Magnitude notation,
- with sign, in Diminished Radix Complement notation,
- with sign, in Radix Complement notation,
- without sign.

1.1 Analysis of the task

My test data will be:

$$(X)_{10} = 2 \longrightarrow (X)_2 = 010$$

$$(Y)_{10} = 4 \longrightarrow (Y)_2 = 100$$

1.2 Sign Magnitude calculations

a) with sign in Sign-Magnitude notation

For $X + Y$

$$z_s = x_s = y_s \longrightarrow z_s = 0$$

$$\begin{array}{r} |X| = 010 \\ |Y| = 100 \\ \hline |Z| = 110 \end{array} \quad \left. \vphantom{\begin{array}{r} |X| = 010 \\ |Y| = 100 \\ \hline |Z| = 110 \end{array}} \right\} +$$

$$(Z)_2^{SM} = 0.110$$

Expected result

For $(-X) + (-Y)$

$$z_s = x_s = y_s \longrightarrow z_s = 1$$

$$\begin{array}{r} |X| = 010 \\ |Y| = 100 \\ \hline |Z| = 110 \end{array} \quad \left. \vphantom{\begin{array}{r} |X| = 010 \\ |Y| = 100 \\ \hline |Z| = 110 \end{array}} \right\} +$$

$$(Z)_2^{SM} = 1.110$$

Expected result

For $X + (-Y)$

$$x_s \neq y_s$$

$$\begin{array}{r} |X| = 010 \\ |\bar{Y}| = 011 \\ \hline |Z| = 101 \end{array} \quad \left. \vphantom{\begin{array}{r} |X| = 010 \\ |\bar{Y}| = 011 \\ \hline |Z| = 101 \end{array}} \right\} +$$

no carry

$$(Z)_2^{SM} = 1.010$$

Expected result

$$z_s = y_s = 1$$

For $(-X) + Y$

$$x_s \neq y_s$$

$$\begin{array}{r} |X| = 010 \\ |\bar{Y}| = 011 \\ \hline |Z| = 101 \end{array} \quad \left. \vphantom{\begin{array}{r} |X| = 010 \\ |\bar{Y}| = 011 \\ \hline |Z| = 101 \end{array}} \right\} +$$

no carry

$$(Z)_2^{SM} = 0.010$$

Expected result

$$z_s = y_s = 0$$

1.2.1 The circuit diagram of Sign-Magnitude Notation adder

 


Figure 1: 4-bit Adder for Sign-Magnitude Notation

1.3 Diminished Radix Complement Calculations

b) with sign, in Diminished Radix Complement notation

$$\begin{array}{rcl}
 \begin{array}{l} (X)_2^{DRC} = 0.010 \\ (Y)_2^{DRC} = 0.100 \\ \hline (Z)_2^{DRC} = 0.110 \end{array} \Bigg\} + & \begin{array}{l} (-X)_2^{DRC} = 1.101 \\ (-Y)_2^{DRC} = 1.011 \\ \hline \begin{array}{c} 1 \leftarrow 1.000 \\ \quad \rightarrow 1 \end{array} \\ \hline (Z)_2^{DRC} = 1.001 \end{array} \Bigg\} + & \begin{array}{l} (-X)_2^{DRC} = 1.101 \\ (-Y)_2^{DRC} = 0.100 \\ \hline \begin{array}{c} 1 \leftarrow 0.001 \\ \quad \rightarrow 1 \end{array} \\ \hline (Z)_2^{DRC} = 0.010 \end{array} \Bigg\} + & \begin{array}{l} (X)_2^{DRC} = 0.010 \\ (-Y)_2^{DRC} = 1.011 \\ \hline (Z)_2^{DRC} = 1.010 \end{array} \Bigg\} + \\
 \text{Expected result} & \text{Expected result} & \text{Expected result} & \text{Expected result}
 \end{array}$$

1.3.1 The circuit diagram of Diminished Radix Complement Notation adder

The 4-bit adder for Diminished Radix Complement notation is as follows:

 


Figure 2: 4-bit Adder for Diminished Radix Complement notation

1.4 Radix Complement Calculations

c) with sign, in Radix Complement notation

$$\begin{array}{rcl}
 \begin{array}{l} (X)_2^{RC} = 0.010 \\ (Y)_2^{RC} = 0.100 \\ \hline (Z)_2^{RC} = 0.110 \end{array} \Bigg\} + & \begin{array}{l} (-X)_2^{RC} = 1.110 \\ (-Y)_2^{RC} = 1.100 \\ \hline \begin{array}{c} \swarrow \leftarrow (Z)_2^{RC} = 1.010 \end{array} \end{array} \Bigg\} + & \begin{array}{l} (-X)_2^{RC} = 1.110 \\ (-Y)_2^{RC} = 0.100 \\ \hline \begin{array}{c} \swarrow \leftarrow (Z)_2^{RC} = 0.010 \end{array} \end{array} \Bigg\} + & \begin{array}{l} (X)_2^{RC} = 0.010 \\ (-Y)_2^{RC} = 1.100 \\ \hline (Z)_2^{RC} = 1.110 \end{array} \Bigg\} + \\
 \text{Expected result} & \text{Expected result} & \text{Expected result} & \text{Expected result}
 \end{array}$$

1.4.1 The circuit diagram of Radix Complement Notation adder

The 4-bit adder for Radix Complement notation is as follows:

 


Figure 3: 4-bit Adder for Radix Complement notation

1.5 Without Sign calculations

d) without sign

$$\begin{array}{r} |X| = 010 \\ |Y| = 100 \\ \hline |Z| = 110 \end{array} \Bigg\}^+$$

Expected result

1.5.1 The circuit diagram of numbers without sign adder

The 4-bit adder for numbers without sign is as follows:

 


Figure 4: 4-bit Adder for unsigned numeric type

This space has been intentionally left blank.

2 Description of the second task

Task 2

Using prepared by yourself test data (pairs of input values and the expected outcomes of the operation), verify the working mode of 4-bit comparator with respect to the used representation of binary numbers, whether it adds numbers:

- with sign, in Sign-Magnitude notation,
- with sign, in Diminished Radix Complement notation,
- with sign, in Radix Complement notation,
- without sign.

2.1 Analysis of the task

My test data will be:

$$(X)_{10} = 2 \longrightarrow (X)_2 = 010$$

$$(Y)_{10} = 4 \longrightarrow (Y)_2 = 100$$

a) with sign in Sign-Magnitude notation

b) with sign, in Diminished Radix Complement notation

Expected result:

$$\left. \begin{array}{l} (X)_2^{SM} = 0.010 \\ (Y)_2^{SM} = 0.100 \end{array} \right\} X < Y$$

$$\left. \begin{array}{l} (-X)_2^{SM} = 1.010 \\ (-Y)_2^{SM} = 1.100 \end{array} \right\} X > Y$$

$$\left. \begin{array}{l} (-X)_2^{SM} = 1.010 \\ (Y)_2^{SM} = 0.100 \end{array} \right\} X < Y$$

$$\left. \begin{array}{l} (X)_2^{SM} = 0.010 \\ (-Y)_2^{SM} = 1.100 \end{array} \right\} X > Y$$

Expected result:

$$\left. \begin{array}{l} (X)_2^{DRC} = 0.010 \\ (Y)_2^{DRC} = 0.100 \end{array} \right\} X < Y$$

$$\left. \begin{array}{l} (-X)_2^{DRC} = 1.101 \\ (-Y)_2^{DRC} = 1.011 \end{array} \right\} X > Y$$

$$\left. \begin{array}{l} (-X)_2^{DRC} = 1.101 \\ (Y)_2^{DRC} = 0.100 \end{array} \right\} X < Y$$

$$\left. \begin{array}{l} (X)_2^{DRC} = 0.010 \\ (-Y)_2^{DRC} = 1.011 \end{array} \right\} X > Y$$

c) with sign, in Radix Complement notation

d) without sign

Expected result:

$$\left. \begin{array}{l} (X)_2^{RC} = 0.010 \\ (Y)_2^{RC} = 0.100 \end{array} \right\} X < Y$$

$$\left. \begin{array}{l} (-X)_2^{RC} = 1.110 \\ (-Y)_2^{RC} = 1.100 \end{array} \right\} X > Y$$

$$\left. \begin{array}{l} (-X)_2^{RC} = 1.110 \\ (Y)_2^{RC} = 0.100 \end{array} \right\} X < Y$$

$$\left. \begin{array}{l} (X)_2^{RC} = 0.010 \\ (-Y)_2^{RC} = 1.100 \end{array} \right\} X > Y$$

Expected result:

$$\left. \begin{array}{l} (X)_2 = 010 \\ (Y)_2 = 100 \end{array} \right\} X < Y$$

2.2 Sign-Magnitude notation comparator circuit diagram

The 4-bit comparator for Sign-Magnitude notation is as follows:

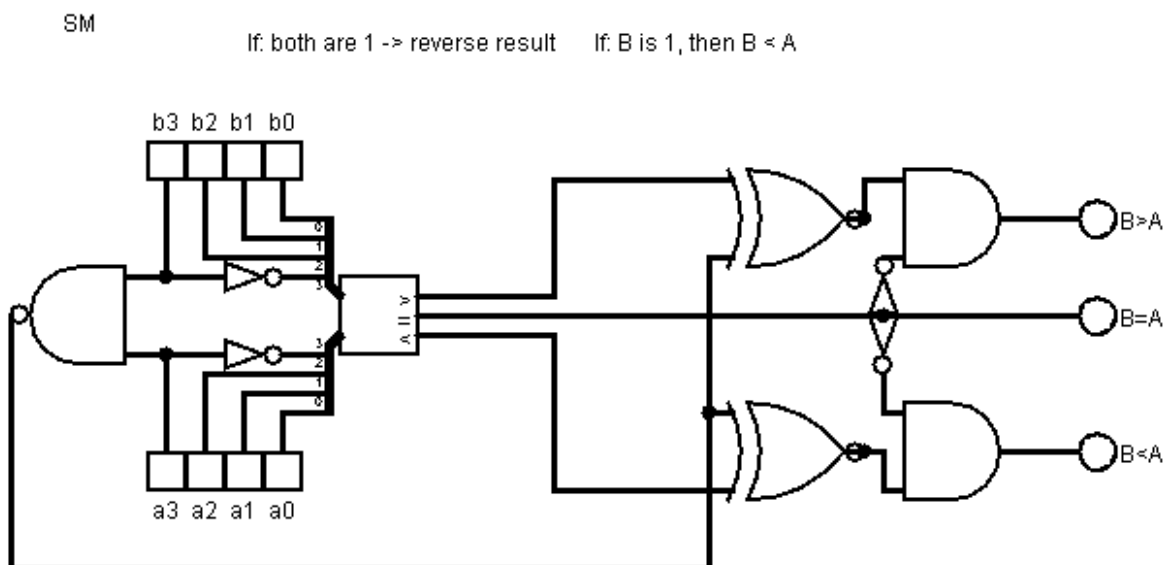


Figure 5: 4-bit comparator for Sign-Magnitude notation

2.3 Diminished Radix Complement comparator circuit diagram

The 4-bit comparator for Diminished Radix Complement notation is as follows:

 


Figure 6: 4-bit comparator for Diminished Radix Complement notation

2.4 Radix Complement notation comparator circuit diagram

The 4-bit comparator for Radix Complement notation is as follows:

 


Figure 7: 4-bit comparator for Radix Complement notation

2.5 Circuit diagram for comparator of numbers without sign

The 4-bit comparator for numbers without sign is as follows:

 


Figure 8: 4-bit comparator for unsigned numeric types

This space has been intentionally left blank.


3 Description of the third task

Task 3

Obtain full 1-bit adder using NAND gates.

3.1 Analysis of the task

The circuit can be presented as follows:

 

3.2 Implementation

We can also very easily imagine and fill a similar Karnaugh grid. Truth Table can be helpful here.

$x_i \ y_i$					
C_i		00	01	11	10
0		00	01	10	01
1		01	10	11	10
		C_{i+1}		S_i	

x_i	y_i	C_i	C_{i+1}	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

And read out individual groups from it:

$x_i \ y_i$					
C_i		00	01	11	10
0		0	0	1	0
1		0	1	1	1
		C_{i+1}		S_i	

$x_i \ y_i$					
C_i		00	01	11	10
0		0	1	0	1
1		1	0	1	0
		C_{i+1}		S_i	

$$C_{i+1} = C_i y_i + x_i y_i + x_i C_i$$

$$S_i = C_i \overline{x_i} \overline{y_i} + \overline{C_i} \overline{x_i} y_i + C_i x_i y_i + \overline{C_i} x_i \overline{y_i}$$


Implementation with NANDS:

$$C_{i+1} = \overline{\overline{C_i} y_i \times \overline{x_i} \overline{y_i} \times x_i C_i}$$

$$S_i = \overline{\overline{C_i} \overline{x_i} \overline{y_i} \times \overline{C_i} \overline{x_i} y_i \times \overline{C_i} x_i y_i \times \overline{C_i} x_i \overline{y_i}}$$

3.3 Circuit diagram

Finally, we get the given circuit:

 


4 Description of the fourth task

Task 4

Obtain full 1-bit subtractor using NAND gates.

 4.1 Analysis of the task

This type of task is even a mirror image of the previous task. The solution is almost the same.



4.2 Implementation

Again, the easiest way to complete the Karnaugh map is with the first filled-in truth table.

$x_i \ y_i$					
B_i		00	01	11	10
0	00	11	00	01	
1	11	10	11	00	
		B_{i+1}		D_i	

x_i	y_i	B_i	B_{i+1}	D_i
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Now we select the groups and we can see that D_i is identical to the summator's S_i , and B_{i+1} is literally a mirror image of the summator's map for C_{i+1} .

$x_i \ y_i$					
B_i		00	01	11	10
0	0	1	0	0	
1	1	1	1	0	
		B_{i+1}		D_i	

$x_i \ y_i$					
B_i		00	01	11	10
0	0	1	0	1	
1	1	0	1	0	
		B_{i+1}		D_i	

$$B_{i+1} = B_i \bar{x}_i + \bar{x}_i y_i + B_i y_i$$

$$D_i = B_i \bar{x}_i \bar{y}_i + \bar{B}_i \bar{x}_i y_i + B_i x_i y_i + \bar{B}_i x_i \bar{y}_i$$


Implementation with NANDS:

$$B_{i+1} = \overline{\overline{B_i} \overline{x_i} \times \overline{x_i} y_i \times \overline{B_i} y_i}$$

$$S_i = \overline{\overline{B_i} \overline{x_i} \overline{y_i} \times \overline{B_i} \overline{x_i} y_i \times \overline{B_i} x_i y_i \times \overline{B_i} x_i \overline{y_i}}$$

4.3 Circuit diagram

Finally, we get the given circuit:

 


5 Description of the fifth task

Task 5

Obtain full 1-bit comparator with comparison starting from the least significant bits.

 5.1 Analysis of the task

Again, let's start the task with a short analysis and a certain graphic representation of the layout



- (1) At this point the circuit thinks that the numbers are equal
- (2) Again, 0 is equal to 0. Circuit still thinks the numbers are equal
- (3) There is no other option for the circuit to know that the overall numbers are not equal. It still assumes that the numbers are equal.
- (4) Finally some numbers differ. As x_4 is 1, and y_4 is 0 the circuit at this moment knows that x is bigger.
- (5) Now we have two equal ones. However, from the previous comparison, the circuit still knows that x is somehow bigger.
- (6) Now y_6 is 1 and x_6 is 0. This means that y is definitely bigger. This is the final comparison.

5.2 Implementation

This time without a truth table and with a short visual representation of the operation of this comparator. This is definitely enough to create a Karnaugh grid.

		G _i E _i L _i							
x _i	y _i	000	001	011	010	110	111	101	100
00		001		010					100
01		001		001					001
11		001		010					100
10		100		100					100

G_{i+1}E_{i+1}L_{i+1}

From this large Karnaugh map we get three Karnaugh maps.

I select the groups and derive the implementation using the AND, and OR gates.

		G _i E _i L _i							
x _i	y _i	000	001	011	010	110	111	101	100
		0	0	0					1
00			0		0				0
01			0		0				0
11			0		0				1
10			1	1	1				1

G_{i+1}

$$G_{i+1} = x_i \bar{y}_i + \bar{y}_i \bar{E}_i \bar{L}_i + x_i \bar{E}_i \bar{L}_i$$

		G _i E _i L _i							
x _i	y _i	000	001	011	010	110	111	101	100
		0		1					0
00			0		0				0
01			0		0				0
11			0		1				0
10			0		0				0

E_{i+1}

$$E_{i+1} = \bar{x}_i \bar{y}_i \bar{G}_i \bar{L}_i + x_i y_i \bar{G}_i \bar{L}_i$$


		G _i E _i L _i							
x _i	y _i	000	001	011	010	110	111	101	100
		1		0					0
00			1		1				1
01			1						0
11			1		0				0
10			0		0				0

L_{i+1}

$$L_{i+1} = \bar{x}_i y_i + \bar{x}_i \bar{G}_i \bar{E}_i + y_i \bar{G}_i \bar{E}_i$$

5.3 Circuit diagram

Finally, we get the given circuit:

 

6 Conclusions

The biggest surprise was definitely the first two tasks - comparators and adders. Definitely their implementation gave a lot of trouble, and left a lot of confusion. However, the rest of the tasks did not seem to be quite problematic - although I made a mistake many times in tasks 3, 4, 5 by connecting the Z_{i+1} outputs to Z_i inputs, which in this matter remain completely independent of each other.