

Digital Circuits Theory - Laboratory						
Academic year	Laboratory exercises on	Mode of studies	Field of studies	Supervisor	Group	Section
2020/2021	Wednesday	SSI	Informatics	KP	1	3
	15:30 – 17:00					

## Report from Exercise No 9

Performed on: 21.10.2020

Exercise Topic: Registers

Performed by:

Dawid Grobert

## Purpose of the exercises

The aim of the classes was to learn about the registers – very useful digital circuits used to store binary information. Using the knowledge about Flip-Flops, and using a few additional combination gates, our task was to prepare digital circuits based on different register patterns, as well as to design several own solutions for the purpose of getting more familiar with the subject.

## 1 Description of the first task

### Task 1

Obtain a 4-bit parallel-in parallel-out register with loading information in one asynchronous stage.

### 1.1 Circuit diagram

During the classes I managed to create a particular digital circuit:

 


Figure 1: Digital circuit made during laboratories

The  $w$  input serves as a kind of "write permission". If  $w$  is set to 1, it allows to change the Flip-Flop values, and if  $w$  is set to 0, it blocks such a change, so that the values are in some way "read-only". When  $w$  is set to 1, the given circuit enters the information from inputs  $x_1, x_2, x_3, x_4$  into the register and the entered information overwrites the previous registered content.

## 2 Description of the second task

### Task 2

Obtain a 4-bit parallel-in parallel-out register with loading information in two asynchronous stages.

Another digital circuit that I managed to prepare had an additional  $Z$  input. It was a fundamental difference between the first task where "loading" of information took place in one asynchronous stage, and here in two asynchronous stages. We can see that it reduced the number of gates by half.

### 2.1 Circuit diagram

 


Figure 2: Digital circuit made during laboratories

This time the  $w$  signal seemed to work in a similar way – it also blocked and allowed writing to the register. The main difference when entering the data was that the data could not be overwritten so easily. The logical ones could no longer be overwritten with zero. This is where the  $Z$  is used, which works in such a way that it resets the saved data by setting all of them to logical zero. Therefore, when entering data, you should first reset the data stored in the Flip-Flop by setting  $Z$  to low and then back to high (as long as you do not want to perform logical OR operations on binary numbers).

### 3 Description of the third task

#### Task 3

Obtain a 4-bit self-setting ring register counter with the effect of “circling 1”.

This time the asynchronous circuit will no longer be built, but the synchronous circuit, with the circulating one. This means that the system should use the clock, and according to the description it should work in the following way:

$$0001 \rightarrow 0010 \rightarrow 0100 \rightarrow 1000 \rightarrow 0001$$

The self-correction system in this case makes sure that setting the wrong initial state of the registry will not cause it to fall out of the correct cycle and thus spoil the operation of the digital system. For example setting 0101 should lead to:

$$0101 \rightarrow 1010 \rightarrow 0100 \rightarrow 1000 \rightarrow 0001$$

#### 3.1 Circuit diagram

 


Figure 3: Digital circuit made during laboratories

#### 3.2 Timing Chart

 


Figure 4: Timing chart of given circuit (see Fig. 3)

## 4 Description of the fourth task

### Task 4

Obtain a 4-bit self-setting ring register counter with the effect of “circling 0”.

This task is very similar to the previous one. The difference is that instead of having a logical one on only one position, and a logical zero on all the others, we have the opposite situation – one logical zero and a logical one on all the others positions.

### 4.1 Circuit diagram

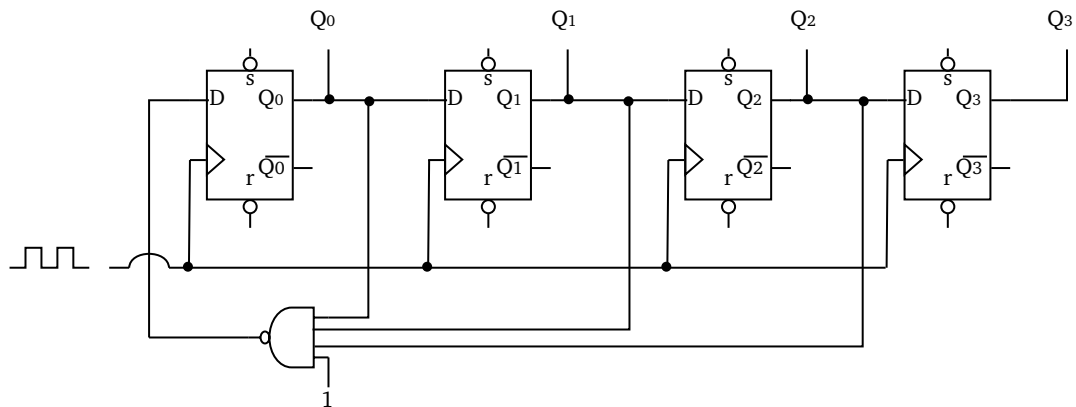


Figure 5: Digital circuit made during laboratories

### 4.2 Timing Chart

 


Figure 6: Timing chart of given circuit (see Fig. 5)

In the previous task the self-correction was not noted on the timing chart, so here the system started from an incorrect configuration so we can analyze how it works.

0001 → 0011 → 0111 → 1110 → 1101 → 1011 → 0111 → 1110

The self-correction is marked in blue. In all aspects, the timing-chart looks like a negated results of a "circling 1".

## 5 Description of the fifth task

### Task 5a

Obtain a 3-bit linear register with the feedback function defined as  $Q_1 \oplus Q_0$

In the case of this task, due to the lack of available XOR gates at the laboratory, it was realized using NAND gates. It took the most time to build the first digital circuit here, because every next part of the task was based only on changing the inputs of our XOR (created with the help of NANDs) so that it would perform XOR operations on the bits we want. The result of this operation always appears at the very beginning of the next output – in this case marked as  $Q_0$ .

Note that in order to perform XOR operations on the  $Q_1$  and  $Q_0$  outputs we connected the inputs of our NANDs specifically to the  $Q_1$ ,  $\overline{Q_0}$ ,  $Q_0$ ,  $\overline{Q_1}$  outputs.



**Warning:** In those tasks, it is also worth mentioning about illegal states that can lead to "spoiling" of the system. For example, setting this specific digital circuit ( $Q_1 \oplus Q_0$ ) to  $Q_0 = 0$ ,  $Q_1 = 0$ , will lead to eternal staying in this state ( $Q_0 = 0$ ,  $Q_1 = 0$ ,  $Q_2 = 0$ ), as  $Q_1 \oplus Q_0$  will always output zero.

### 5.1 Circuit diagram

 


Figure 7: Digital circuit made during laboratories

### 5.2 Timing Chart

 


Figure 8: Timing chart of given circuit (see Fig. 7), and table showing exemplary values on the output

### Task 5b

Obtain a 3-bit linear register with the feedback function defined as  $Q_2 \oplus Q_0$

The circuit was almost unchanged compared to the previous task. Similarly, to perform the XOR operations for  $Q_2$ , and  $Q_0$  we used the outputs  $Q_2$ ,  $\overline{Q_0}$ ,  $Q_0$ ,  $\overline{Q_2}$ , to connect the NANDs.

It is also worth adding that here an illegal setting would be  $Q_0 = 0$ ,  $Q_1 = 0$ ,  $Q_2 = 0$ . This setting would last forever.

### 5.3 Circuit diagram

 


Figure 9: Digital circuit made during laboratories

### 5.4 Timing Chart

 


Figure 10: Timing chart of given circuit (see Fig. 9), and table showing exemplary values on the output

### Task 5c

Obtain a 3-bit linear register with the feedback function defined as  $Q_2 \oplus Q_1$

Again, the only change that has been made is the connection of NAND gates, which have to simulate XOR operation for  $Q_2$  and  $Q_1$ . To achieve this, their inputs have been connected – no surprise, to the inputs:  $Q_2, \overline{Q_1}, \overline{Q_2}$  and  $Q_1$ .

Here again, it would be wrong to set values:  $Q_0 = 0, Q_1 = 0, Q_2 = 0$ . This is an illegal state.

## 5.5 Circuit diagram

 


Figure 11: Digital circuit made during laboratories

## 5.6 Timing Chart

 


Figure 12: Timing chart of given circuit (see Fig. 11), and table showing exemplary values on the output

## 6 Conclusions

Luckily, all the tasks were completed in the laboratory. From the very beginning, when I was creating a digital circuit from Task 5 (see page 5), I completely forgot about the illegal states that can spoil it. It is important to be careful and vigilant about building digital circuits. Most of the tasks were carried out without any major problems, and the proper organization of work and cables in Task 5 allowed for quick realization of the next sub-tasks.